

Roll No. ....

Subject Code—6800

**M.C.A. (Second Year) EXAMINATION**

(5 Years Integrated Course (D.E.)

(Main Batch 2009)

**DIGITAL ELECTRONICS**

**MCA-203**

*Time : 3 Hours*

*Maximum Marks : 70*

**Note :** Attempt any *Five* questions. All questions carry equal marks.

1. (a) Realise AND gate and OR gates with the help of NAND gates only.
- (b) Realise EX-OR gate with the help of four NAND gates only.
- (c) State and prove deMorgan's theorem.

2. (a) Explain the process of converting the following :
  - (i) Octal to Binary
  - (ii) Decimal to Octal
  - (iii) Hexadecimal to Binary.
- (b) Explain the process for signed number addition and subtraction.
- (c) What are error codes ? Explain.
3. (a) What are Min Terms and Max Terms\* ?
- (b) Draw and explain the circuit for Full Adder.
- (c) What is Don't Case Condition ?
4. (a) Design a Gray to Binary Code converter.
- (b) Realize using NAND gates only :
 
$$f(A, B, C, D) = \Sigma (1, 2, 3, 5, 9, 11, 13) + d (4, 8, 12)$$
5. (a) Convert S.R. flip flop to J.K. flip flop using design methodology.
- (b) What is Race Around Condition ? How can it be rectified ?

6. (a) Explain how Universal Shift Register works.  
(b) Explain the working of Bidirectional Shift Register.
7. (a) Design a MOD-7 counter.  
(b) Differentiate between Ripple and Synchronous Counter.
8. Write short notes on the following :
  - (a) TTL NAND Gate
  - (b) Characteristics of Digital IC's.